


# CHAPTER 5-2

The Processor

---

By Pattama Longani  
Collage of arts, media and Technology


# DATAPATHS

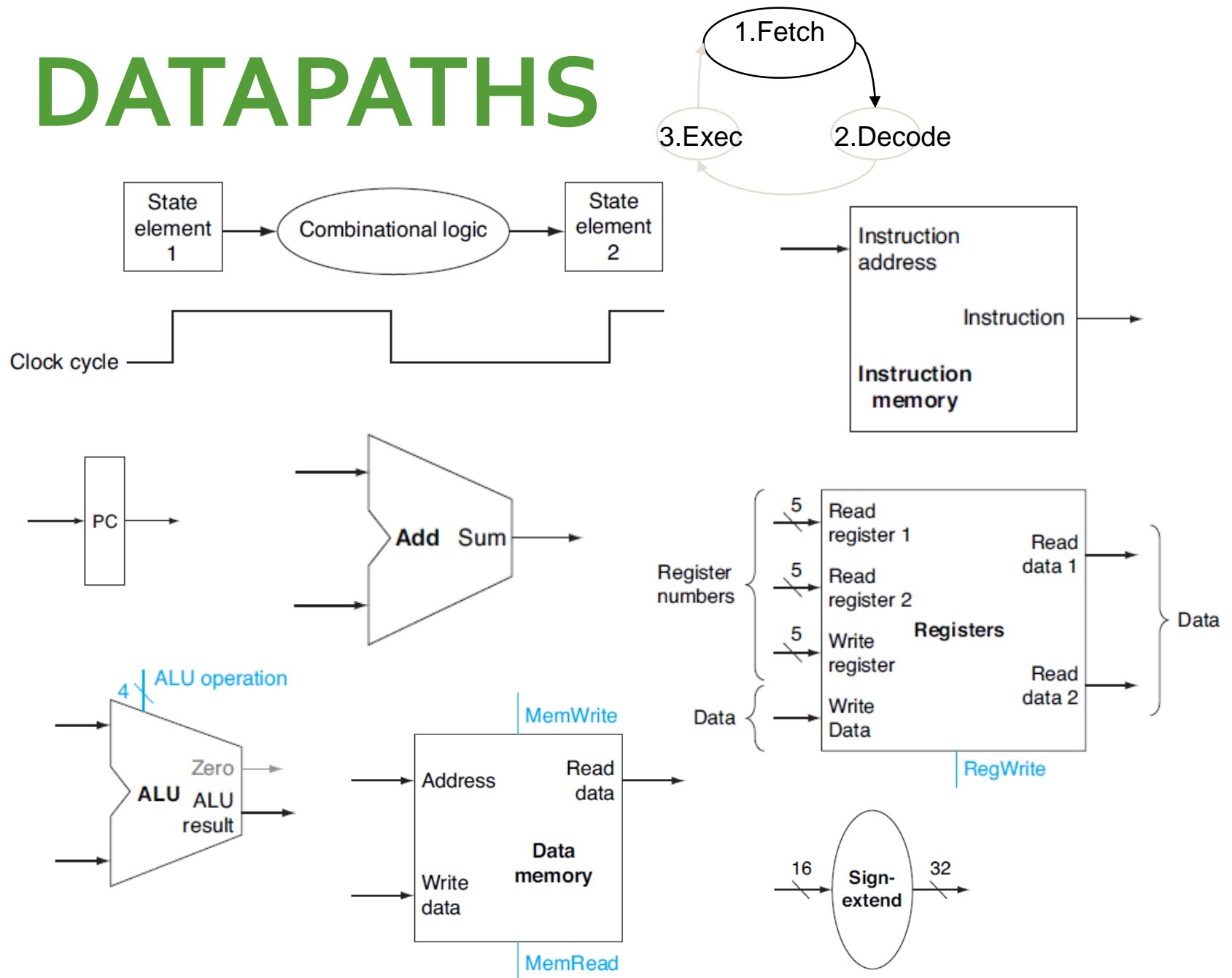

# COMBINATIONAL ELEMENTS


- AND-gate

- $Y = A \& B$

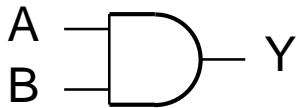


- Adder

- $Y = A + B$

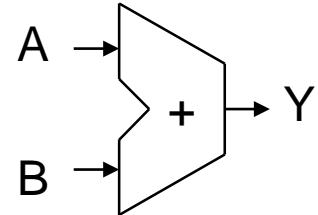


- Multiplexer

- $Y = 0 ? 0 : 1$

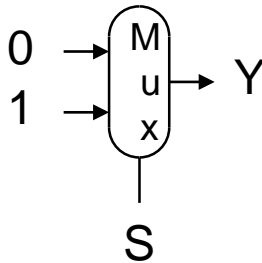

- Arithmetic/Logic Unit

- $Y = F(A, B)$

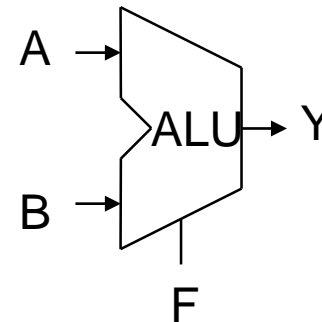

In this section, we use **MIPS subset** to build simple implementation using the datapath of the last section and adding a simple control function

op	rs	rt	rd	shamt	funct
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

Field	0	rs	rt	rd	shamt	funct
Bit positions	31:26	25:21	20:16	15:11	10:6	5:0

a. R-type instruction


Field	35 or 43	rs	rt	address
Bit positions	31:26	25:21	20:16	15:0

b. Load or store instruction

Field	4	rs	rt	address
Bit positions	31:26	25:21	20:16	15:0

c. Branch instruction


op	rs	rt	constant or address
6 bits	5 bits	5 bits	16 bits

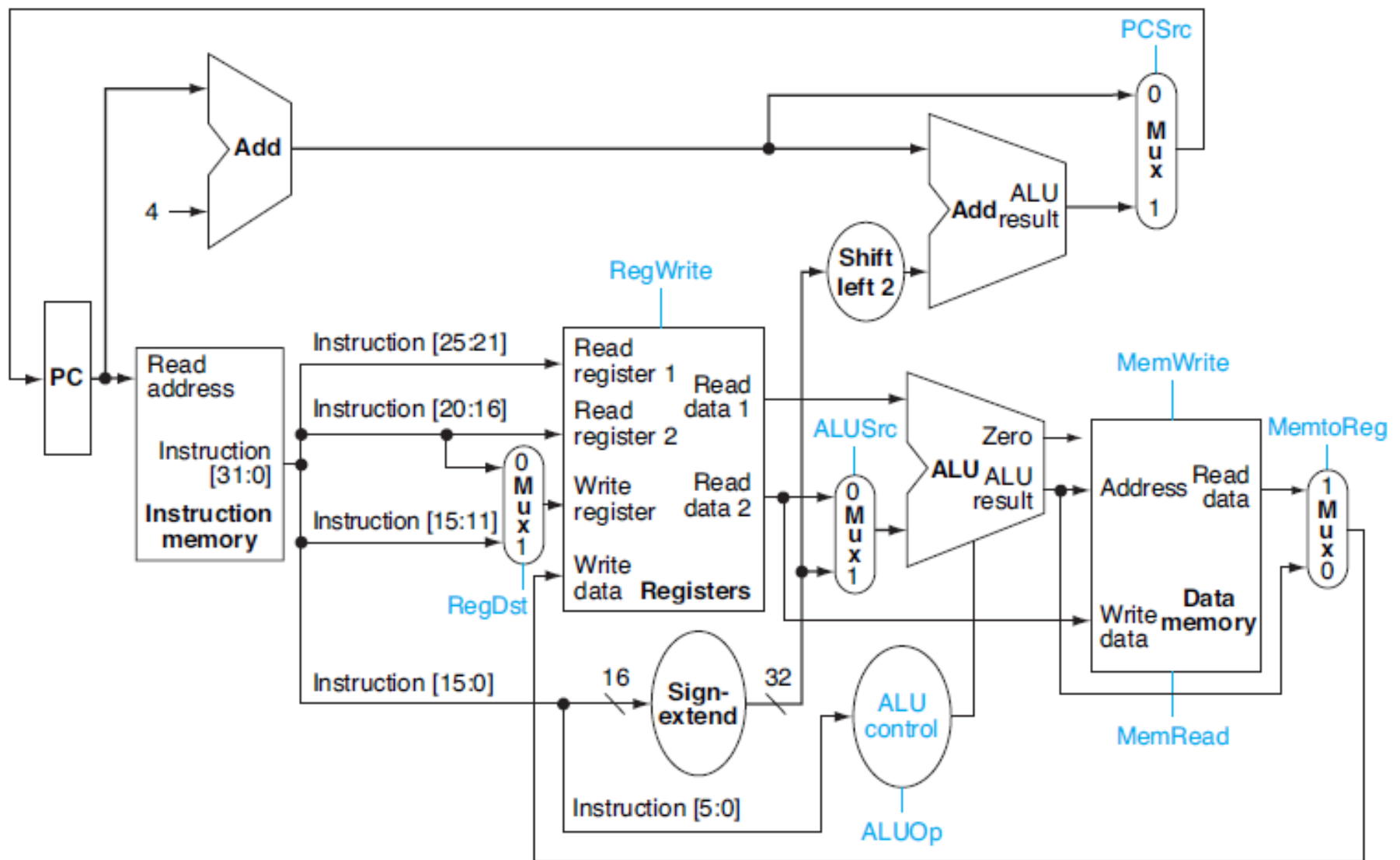

0	rs	rt	rd	shamt	funct
31:26	25:21	20:16	15:11	10:6	5:0

35 or 43	rs	rt	address
31:26	25:21	20:16	15:0

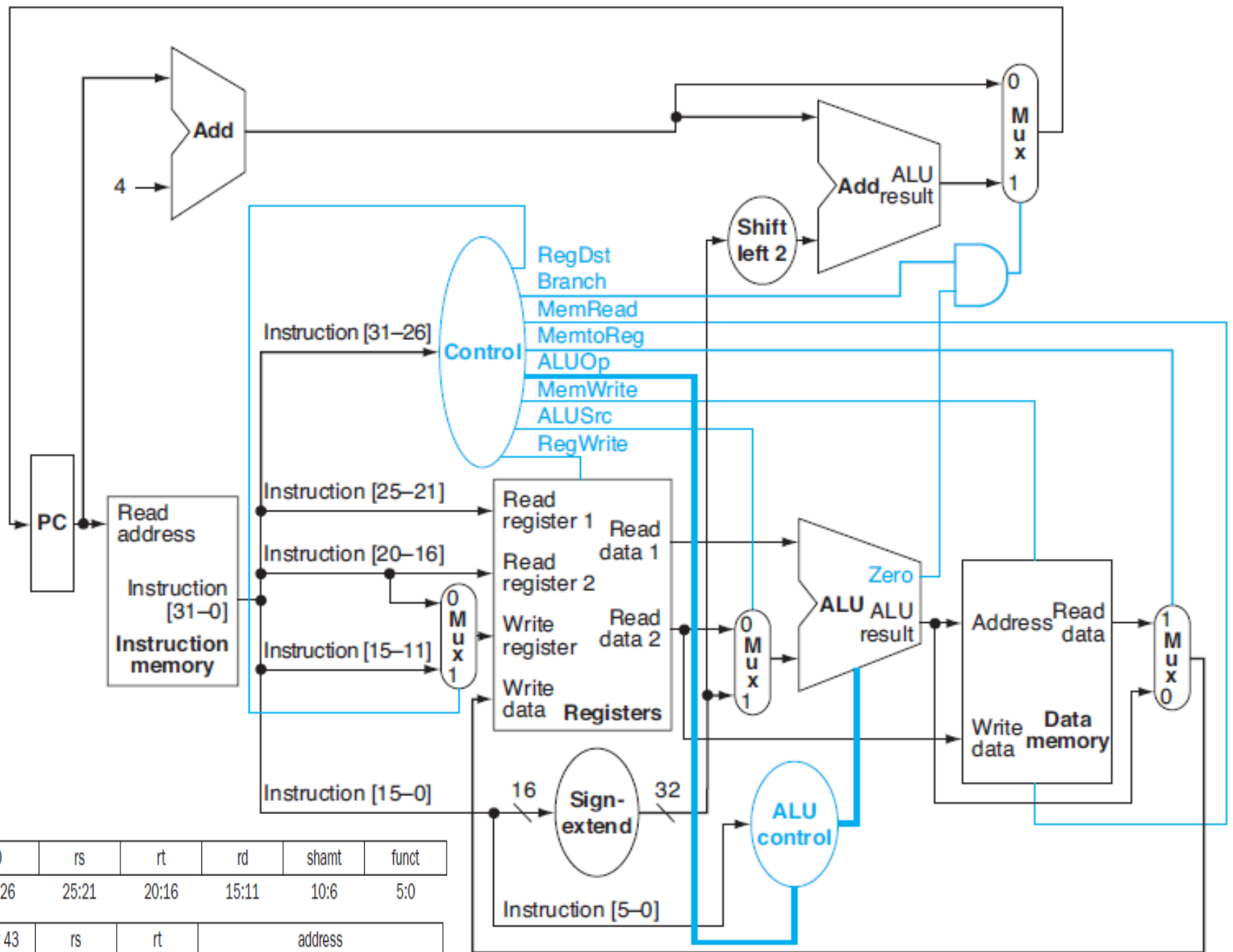

# FOUR CONTROL INPUTS OF ALU

ALU control lines	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	set on less than
1100	NOR

- For load word and store word instructions, we use the ALU to compute the memory address by addition



Instruction opcode	ALUOp	Instruction operation	Funct field	Desired ALU action	ALU control input
LW	00	load word	XXXXXX	add	0010
SW	00	store word	XXXXXX	add	0010
Branch equal	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
R-type	10	subtract	100010	subtract	0110
R-type	10	AND	100100	AND	0000
R-type	10	OR	100101	OR	0001
R-type	10	set on less than	101010	set on less than	0111

ALUOp indicates whether the operation to be performed should be

- ❖ add (00) : for loads and stores,
- ❖ subtract (01) : for beq,
- ❖ determined by the operation
- ❖ encoded in the funct field (10) : R-type instruction

# MIPS Reference Data

①



## CORE INSTRUCTION SET

NAME, MNEMONIC	FOR-MAT	OPERATION (in Verilog)	OPCODE / FUNCT (Hex)
Add	add R	$R[rd] = R[rs] + R[rt]$	(1) 0/20 <sub>hex</sub>
Add Immediate	addi I	$R[rt] = R[rs] + \text{SignExtImm}$	(1,2) 8 <sub>hex</sub>
Add Imm. Unsigned	addiu I	$R[rt] = R[rs] + \text{SignExtImm}$	(2) 9 <sub>hex</sub>
Add Unsigned	addu R	$R[rd] = R[rs] + R[rt]$	0/21 <sub>hex</sub>
And	and R	$R[rd] = R[rs] \& R[rt]$	0/24 <sub>hex</sub>
And Immediate	andi I	$R[rt] = R[rs] \& \text{ZeroExtImm}$	(3) c <sub>hex</sub>
Branch On Equal	beq I	if( $R[rs] == R[rt]$ ) $PC = PC + 4 + \text{BranchAddr}$	(4) 4 <sub>hex</sub>
Branch On Not Equal	bne I	if( $R[rs] != R[rt]$ ) $PC = PC + 4 + \text{BranchAddr}$	(4) 5 <sub>hex</sub>
Jump	j J	$PC = \text{JumpAddr}$	(5) 2 <sub>hex</sub>
Jump And Link	jal J	$R[31] = PC + 8; PC = \text{JumpAddr}$	(5) 3 <sub>hex</sub>
Jump Register	jr R	$PC = R[rs]$	0/08 <sub>hex</sub>
Load Byte Unsigned	lbu I	$R[rt] = \{24'b0, M[R[rs] + \text{SignExtImm}](7:0)\}$	(2) 24 <sub>hex</sub>
Load Halfword Unsigned	lhu I	$R[rt] = \{16'b0, M[R[rs] + \text{SignExtImm}](15:0)\}$	(2) 25 <sub>hex</sub>
Load Linked	ll I	$R[rt] = M[R[rs] + \text{SignExtImm}]$	(2,7) 30 <sub>hex</sub>
Load Upper Imm.	lui I	$R[rt] = \{\text{imm}, 16'b0\}$	f <sub>hex</sub>
Load Word	lw I	$R[rt] = M[R[rs] + \text{SignExtImm}]$	(2) 23 <sub>hex</sub>
Nor	nor R	$R[rd] = \sim(R[rs]   R[rt])$	0/27 <sub>hex</sub>
Or	or R	$R[rd] = R[rs]   R[rt]$	0/25 <sub>hex</sub>
Or Immediate	ori I	$R[rt] = R[rs]   \text{ZeroExtImm}$	(3) d <sub>hex</sub>
Set Less Than	slt R	$R[rd] = (R[rs] < R[rt]) ? 1 : 0$	0/2a <sub>hex</sub>
Set Less Than Imm.	slti I	$R[rt] = (R[rs] < \text{SignExtImm}) ? 1 : 0$	(2) a <sub>hex</sub>
Set Less Than Imm. Unsigned	sltiu I	$R[rt] = (R[rs] < \text{SignExtImm}) ? 1 : 0$	(2,6) b <sub>hex</sub>
Set Less Than Unsig.	sltu R	$R[rd] = (R[rs] < R[rt]) ? 1 : 0$	(6) 0/2b <sub>hex</sub>
Shift Left Logical	sll R	$R[rd] = R[rt] \ll \text{shamt}$	0/00 <sub>hex</sub>

## ARITHMETIC CORE INSTRUCTION SET

②

OPCODE / FMT / FT / FUNCT (Hex)

NAME, MNEMONIC	FOR-MAT	OPERATION	OPCODE / FMT / FT / FUNCT (Hex)
Branch On FP True	bc1t FI	if(FPcond) $PC = PC + 4 + \text{BranchAddr}$	(4) 11/8/1/--
Branch On FP False	bc1f FI	if(!FPcond) $PC = PC + 4 + \text{BranchAddr}$	(4) 11/8/0/--
Divide	div R	$Lo = R[rs] / R[rt]; Hi = R[rs] \% R[rt]$	0/--/1a
Divide Unsigned	divu R	$Lo = R[rs] / R[rt]; Hi = R[rs] \% R[rt]$	(6) 0/--/1b
FP Add Single	add.s FR	$F[fd] = F[fs] + F[ft]$	11/10/--/0
FP Add Double	add.d FR	$\{F[fd], F[fd+1]\} = \{F[fs], F[fs+1]\} + \{F[ft], F[ft+1]\}$	11/11/--/0
FP Compare Single	c.x.s* FR	$FPcond = (F[fs] \text{ op } F[ft]) ? 1 : 0$	11/10/--/y
FP Compare Double	c.x.d* FR	$FPcond = (\{F[fs], F[fs+1]\} \text{ op } \{F[ft], F[ft+1]\}) ? 1 : 0$ * (x is eq, lt, or le) (op is ==, <, or <=) (y is 32, 3c, or 3e)	11/11/--/y
FP Divide Single	div.s FR	$F[fd] = F[fs] / F[ft]$	11/10/--/3
FP Divide Double	div.d FR	$\{F[fd], F[fd+1]\} = \{F[fs], F[fs+1]\} / \{F[ft], F[ft+1]\}$	11/11/--/3
FP Multiply Single	mul.s FR	$F[fd] = F[fs] * F[ft]$	11/10/--/2
FP Multiply Double	mul.d FR	$\{F[fd], F[fd+1]\} = \{F[fs], F[fs+1]\} * \{F[ft], F[ft+1]\}$	11/11/--/2
FP Subtract Single	sub.s FR	$F[fd] = F[fs] - F[ft]$	11/10/--/1
FP Subtract Double	sub.d FR	$\{F[fd], F[fd+1]\} = \{F[fs], F[fs+1]\} - \{F[ft], F[ft+1]\}$	11/11/--/1
Load FP Single	lwc1 I	$F[rt] = M[R[rs] + \text{SignExtImm}]$	(2) 31/--/1--
Load FP Double	ldc1 I	$F[rt] = M[R[rs] + \text{SignExtImm}]; F[rt+1] = M[R[rs] + \text{SignExtImm} + 4]$	(2) 35/--/1--
Move From Hi	mfhi R	$R[rd] = Hi$	0/--/10
Move From Lo	mflo R	$R[rd] = Lo$	0/--/12
Move From Control	mfc0 R	$R[rd] = CR[rs]$	10/0/--/0
Multiply	mult R	$\{Hi, Lo\} = R[rs] * R[rt]$	0/--/18
Multiply Unsigned	multu R	$\{Hi, Lo\} = R[rs] * R[rt]$	(6) 0/--/19
Shift Right Arith.	sra R	$R[rd] = R[rt] \gg \text{shamt}$	0/--/3
Store FP Single	swc1 I	$M[R[rs] + \text{SignExtImm}] = F[rt]$	(2) 39/--/1--
Store FP Double	sdc1 I	$M[R[rs] + \text{SignExtImm}] = F[rt]; M[R[rs] + \text{SignExtImm} + 4] = F[rt+1]$	(2) 3d/--/1--

## FLOATING-POINT INSTRUCTION FORMATS

FR	opcode	fmt	ft	fs	fd	funct
	31	26 25	21 20	16 15	11 10	6 5 0
FI	opcode	fmt	ft	immediate		
	31	26 25	21 20	16 15		

- Note that: R-type instructions works according to the function code part.



Instruction opcode	ALUOp	Instruction operation	Funct field	Desired ALU action	ALU control input
LW	00	load word	XXXXXX	add	0010
SW	00	store word	XXXXXX	add	0010
Branch equal	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
R-type	10	subtract	100010	subtract	0110
R-type	10	AND	100100	AND	0000
R-type	10	OR	100101	OR	0001
R-type	10	set on less than	101010	set on less than	0111

X= don't care term

ALUOp		Funct field						Operation
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0	
0	0	X	X	X	X	X	X	0010
0	1	X	X	X	X	X	X	0110
1	0	X	X	0	0	0	0	0010
1	X	X	X	0	0	1	0	0110
1	0	X	X	0	1	0	0	0000
1	0	X	X	0	1	0	1	0001
1	X	X	X	1	0	1	0	0111
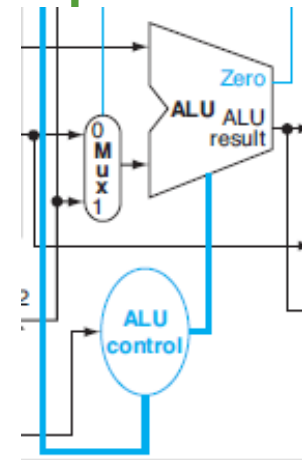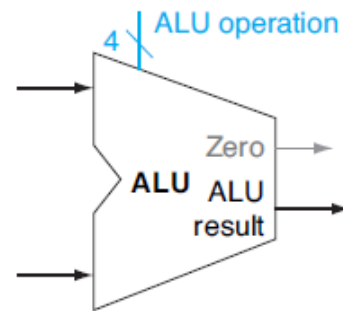
# ALU CONTROL

- **ALUOp** indicates whether the operation to be performed should be
  - 00 = add
  - 01 = sub
  - 10 = function field



ALUOp		Funct field						Operation
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0	
0	0	X	X	X	X	X	X	0010
0	1	X	X	X	X	X	X	0110
1	0	X	X	0	0	0	0	0010
1	X	X	X	0	0	1	0	0110
1	0	X	X	0	1	0	0	0000
1	0	X	X	0	1	0	1	0001
1	X	X	X	1	0	1	0	0111


0

1

Signal name	Effect when deasserted	Effect when asserted
RegDst	The register destination number for the Write register comes from the <b>rt</b> field (bits 20:16).	The register destination number for the Write register comes from the <b>rd</b> field (bits 15:11).
RegWrite	None.	The register on the Write register input is written with the value on the Write data input.
ALUSrc	The second ALU operand comes from the second register file output (Read data 2).	The second ALU operand is the sign-extended, lower 16 bits of the instruction.
PCSrc	The PC is replaced by the output of the adder that computes the value of <b>PC + 4</b> .	The PC is replaced by the output of the adder that computes the <b>branch target</b> .
MemRead	None.	Data memory contents designated by the address input are put on the Read data output.
MemWrite	None.	Data memory contents designated by the address input are replaced by the value on the Write data input.
MemtoReg	The value fed to the register <b>Write data</b> input comes from the ALU.	The value fed to the register <b>Write data</b> input comes from the data memory.

## Control

Instruction	RegDst	ALUSrc	Memto-Reg	Reg-Write	Mem-Read	Mem-Write	Branch	ALUOp1	ALUOp0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

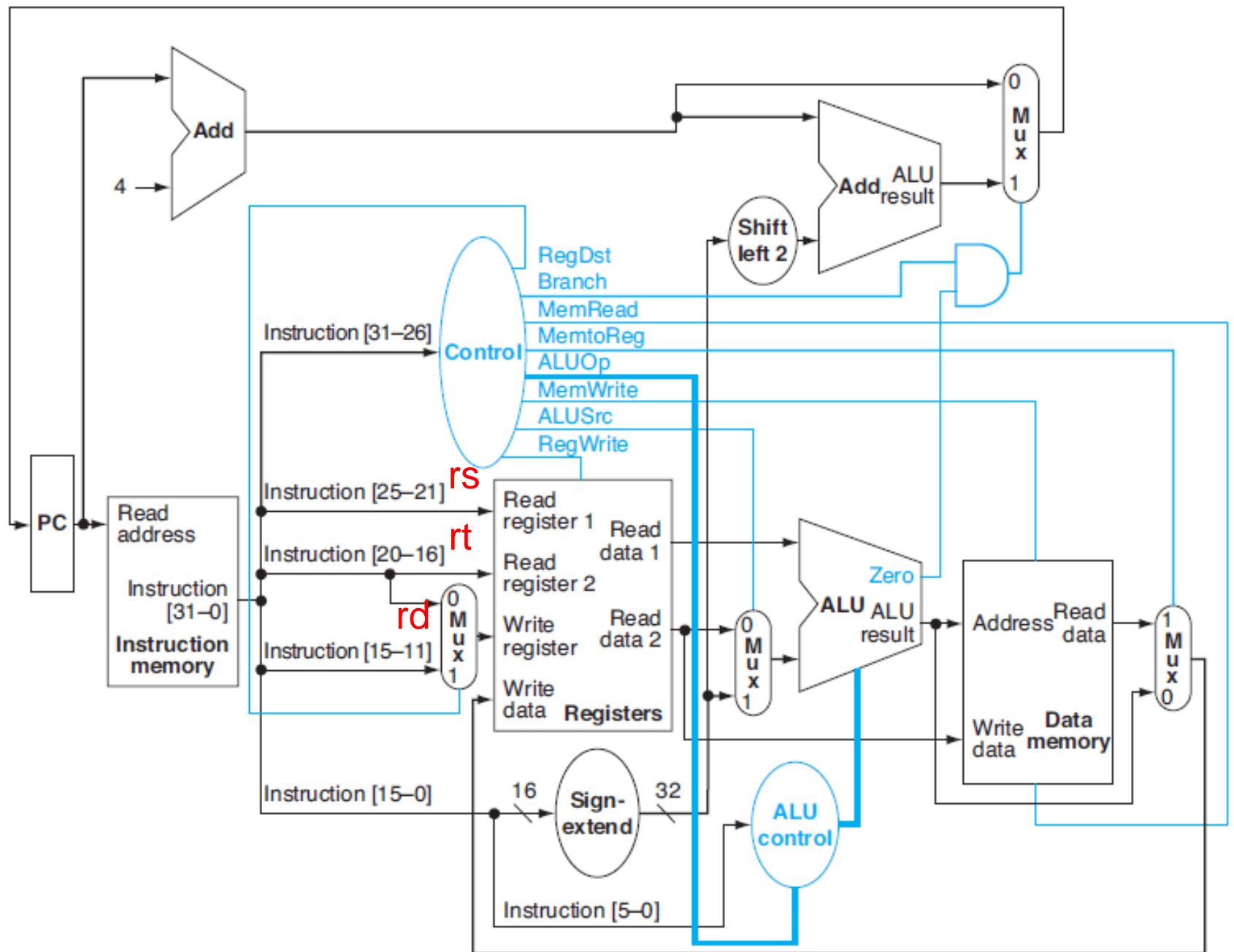

35<sub>ten</sub>43<sub>ten</sub>4<sub>ten</sub>

Input or output	Signal name	R-format	lw	sw	beq
Inputs	Op5	0	1	1	0
	Op4	0	0	0	0
	Op3	0	0	1	0
	Op2	0	0	0	1
	Op1	0	1	1	0
	Op0	0	1	1	0
Outputs	RegDst	1	0	X	X
	ALUSrc	0	1	1	0
	MemtoReg	0	1	X	X
	RegWrite	1	1	0	0
	MemRead	0	1	0	0
	MemWrite	0	0	1	0
	Branch	0	0	0	1
	ALUOp1	1	0	0	0
	ALUOp0	0	0	0	1

00 = add

01 = sub

10 = function field

# ADD = R-TYPE

Input or output	Signal name	R-format	lw	sw	beq
Inputs	Op5	0	1	1	0
	Op4	0	0	0	0
	Op3	0	0	1	0
	Op2	0	0	0	1
	Op1	0	1	1	0
	Op0	0	1	1	0
Outputs	RegDst	1	0	X	X
	ALUSrc	0	1	1	0
	MemtoReg	0	1	X	X
	RegWrite	1	1	0	0
	MemRead	0	1	0	0
	MemWrite	0	0	1	0
	Branch	0	0	0	1
	ALUOp1	1	0	0	0
	ALUOp0	0	0	0	1

**ALUOp 10 = function field**


000000

32<sub>10</sub> = 1000000

op	rs	rt	rd	shamt	funct
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits



# ADD = R-TYPE

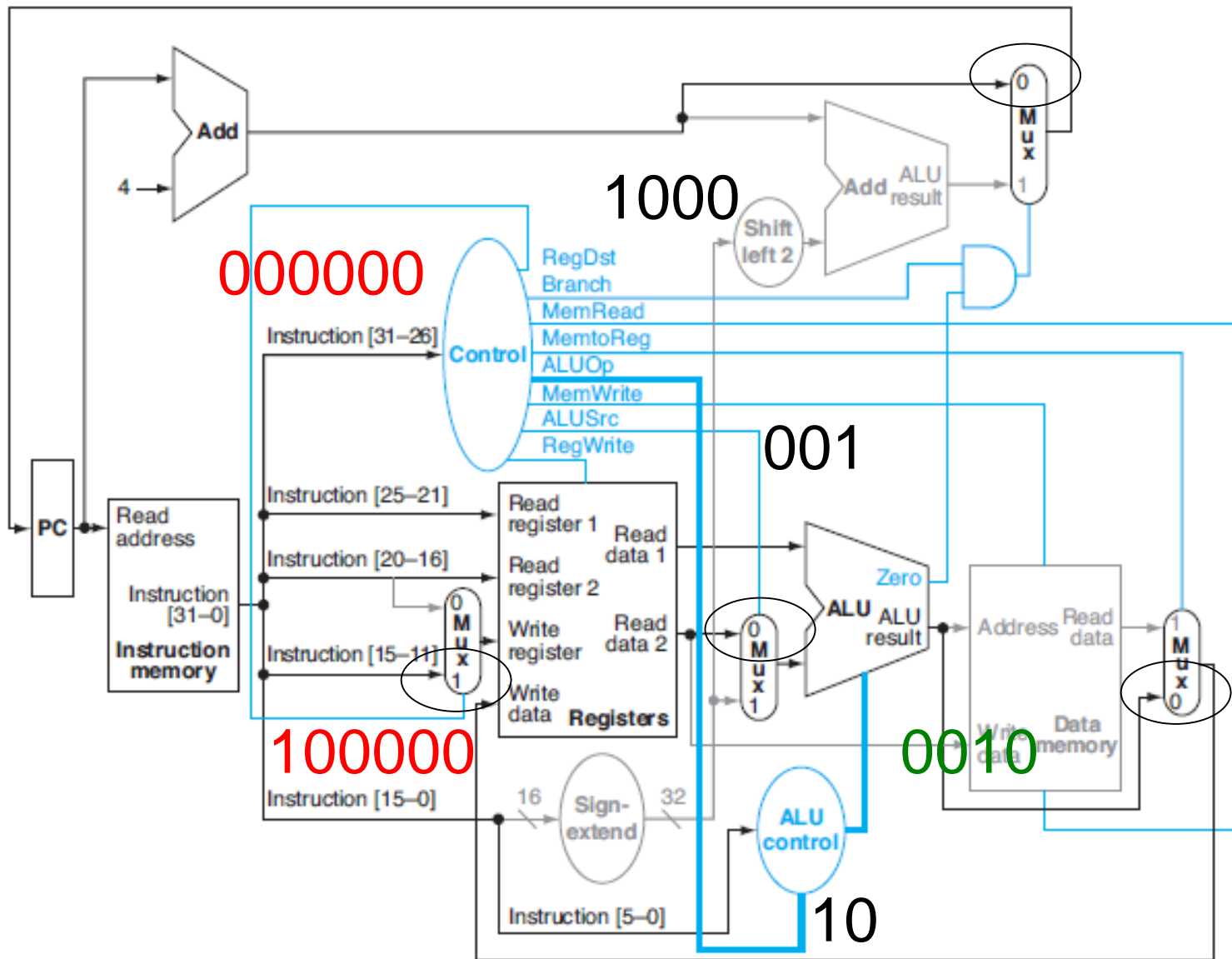


# Load = I-Type

Input or output	Signal name	R-format	lw	sw	beq
Inputs	Op5	0	1	1	0
	Op4	0	0	0	0
	Op3	0	0	1	0
	Op2	0	0	0	1
	Op1	0	1	1	0
	Op0	0	1	1	0
Outputs	RegDst	1	0	X	X
	ALUSrc	0	1	1	0
	MemtoReg	0	1	X	X
	RegWrite	1	1	0	0
	MemRead	0	1	0	0
	MemWrite	0	0	1	0
	Branch	0	0	0	1
	ALUOp1	1	0	0	0
	ALUOp0	0	0	0	1

**ALUOp 00 = add**

100011

op	rs	rt	constant or address
6 bits	5 bits	5 bits	16 bits

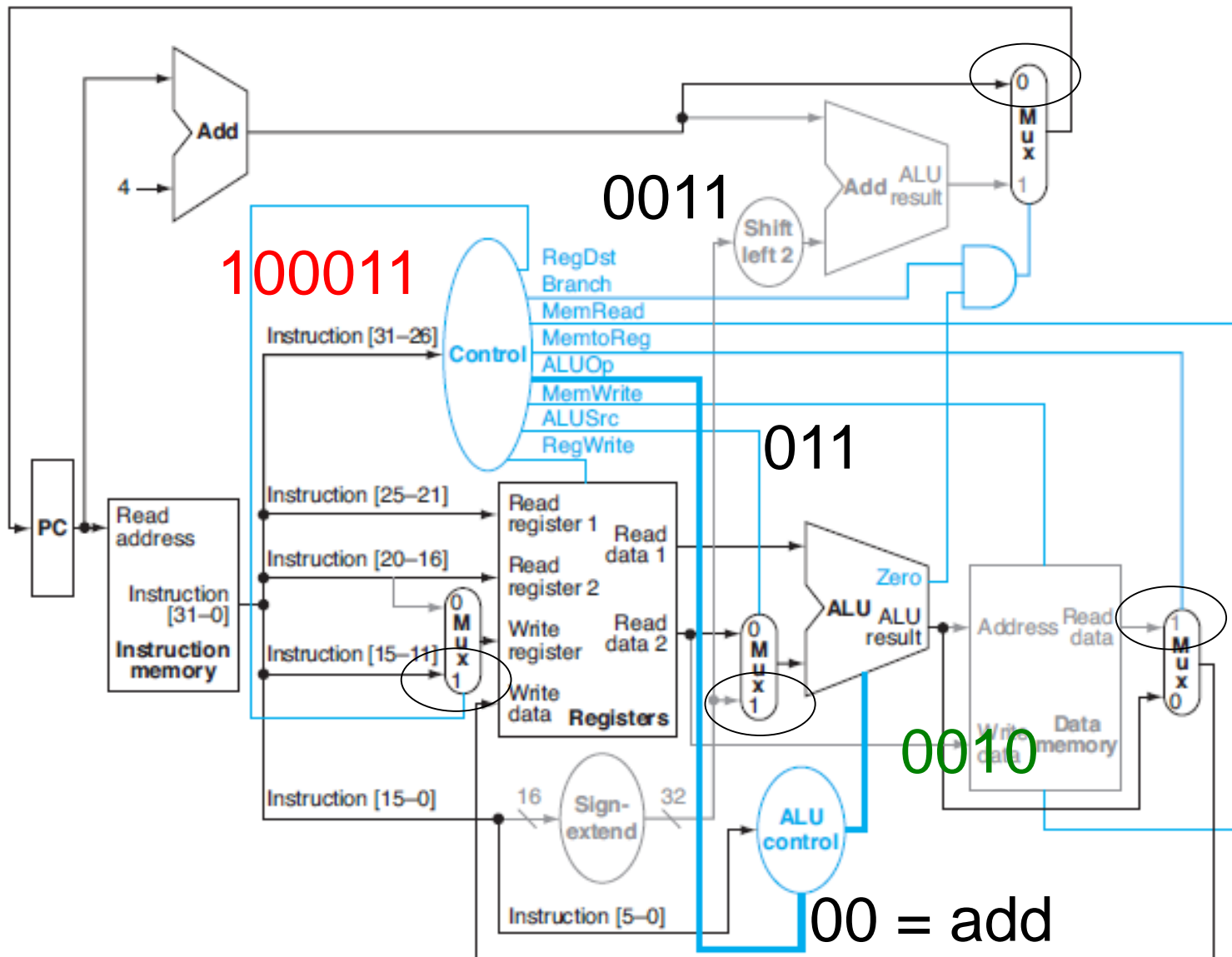

# SINGLE-CYCLE IMPLEMENTATION


- everything occurs in one clock cycle
- There are four steps to execute the instruction; (ordered by the flow of information)

## **EXAMPLE** : add \$s1 \$s2 \$s3

1. The instruction is fetched, and the PC is incremented.
2. Two registers, \$s2 and \$s3, are read from the register file; also, the main control unit computes the setting of the control lines during this step.

3. The ALU operates on the data read from the register file, using the function code (bits 5:0, which is the funct field, of the instruction) to generate the ALU function.

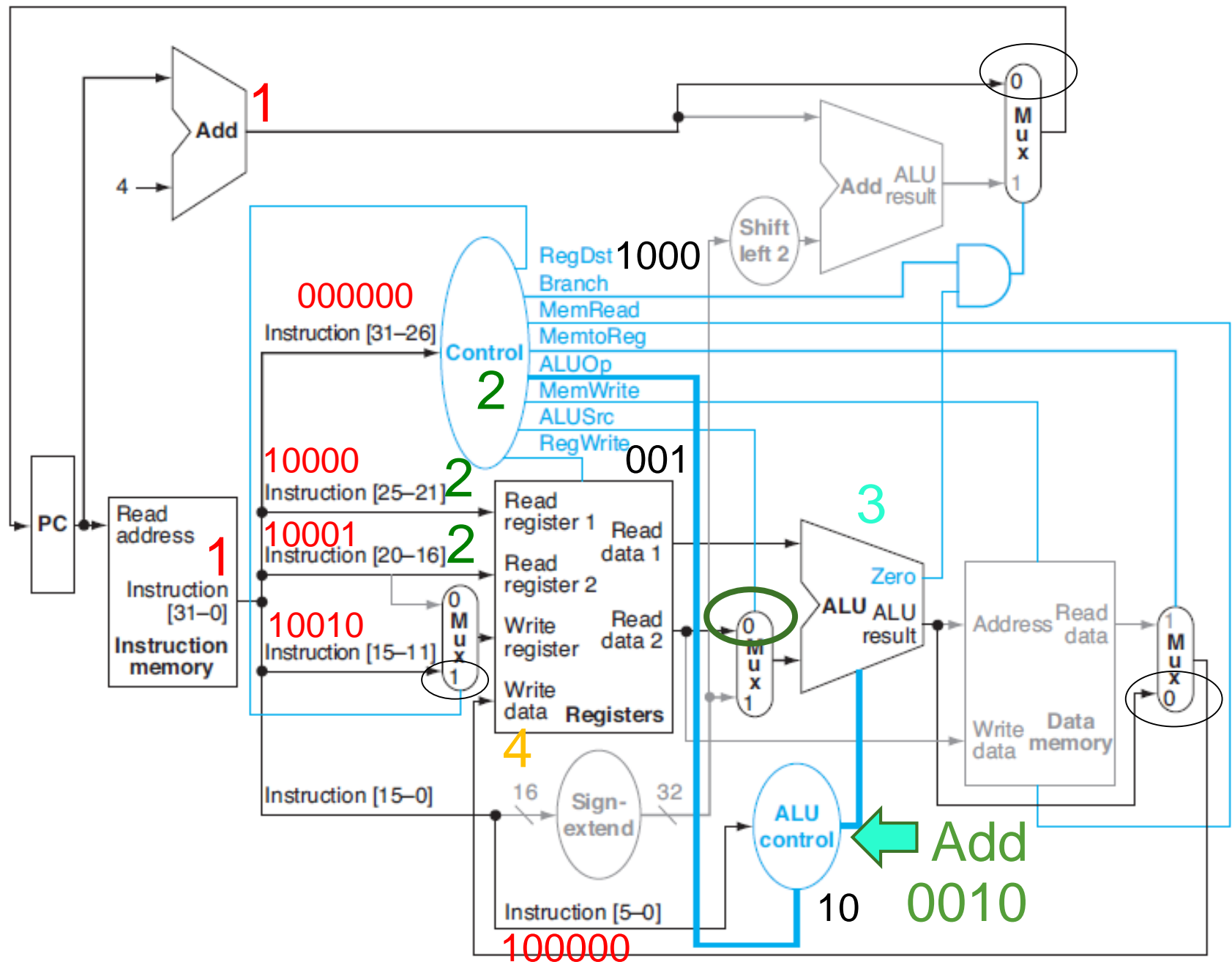
4. The result from the ALU is written into the register file using bits 15:11 of the instruction to select the destination register (\$s1).



## EXAMPLE : lw \$t1, offset(\$t2)

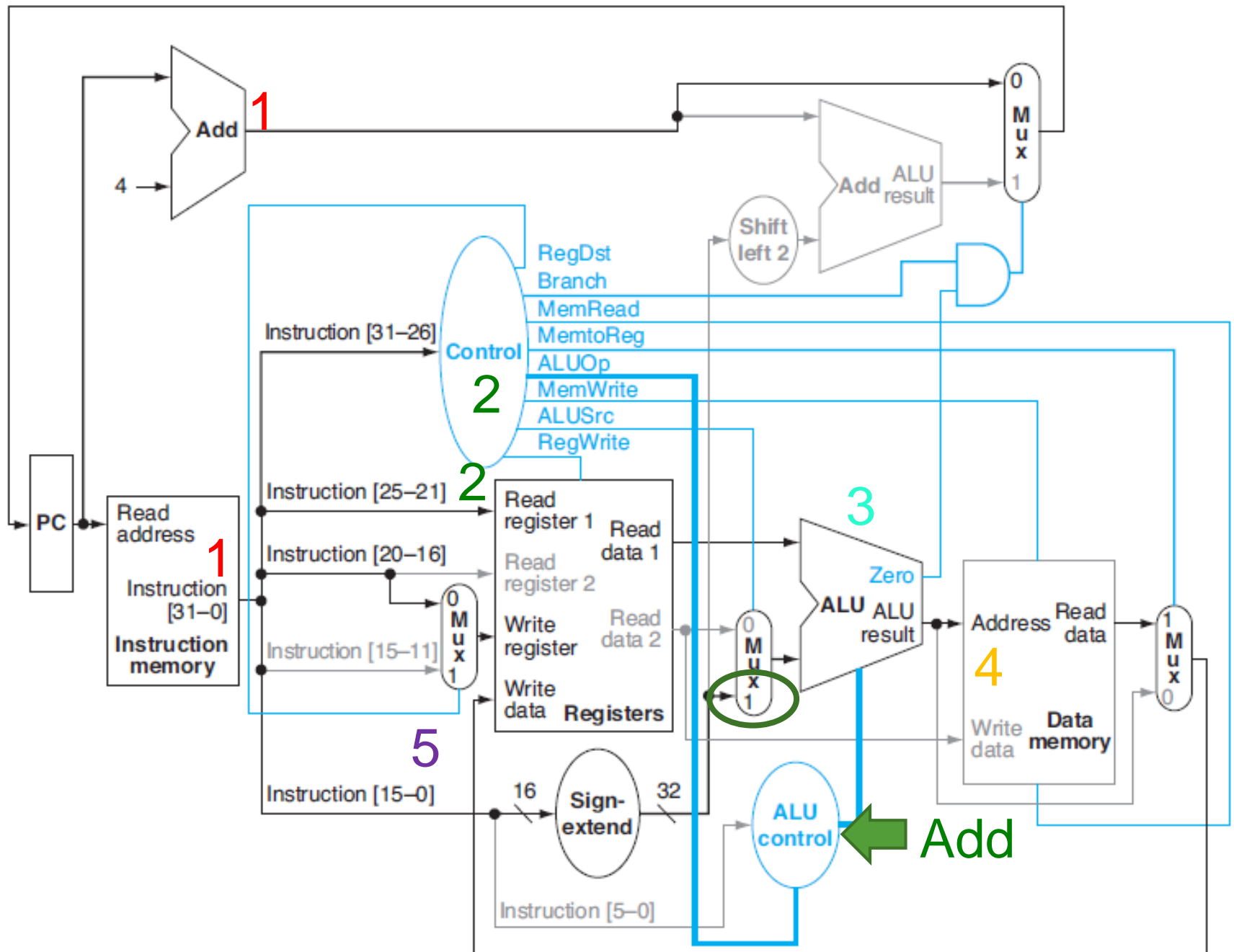
1. An instruction is fetched from the instruction memory, and the PC is incremented.
2. A register (\$t2) value is read from the register file.
3. The ALU computes the sum of the value read from the register file and the sign-extended, lower 16 bits of the instruction (offset).
4. The sum from the ALU is used as the address for the data memory.
5. The data from the memory unit is written into the register file; the register destination is given by bits 20:16 of the instruction (\$t1) .






## **EXAMPLE : beq \$t1,\$t2,offset,**

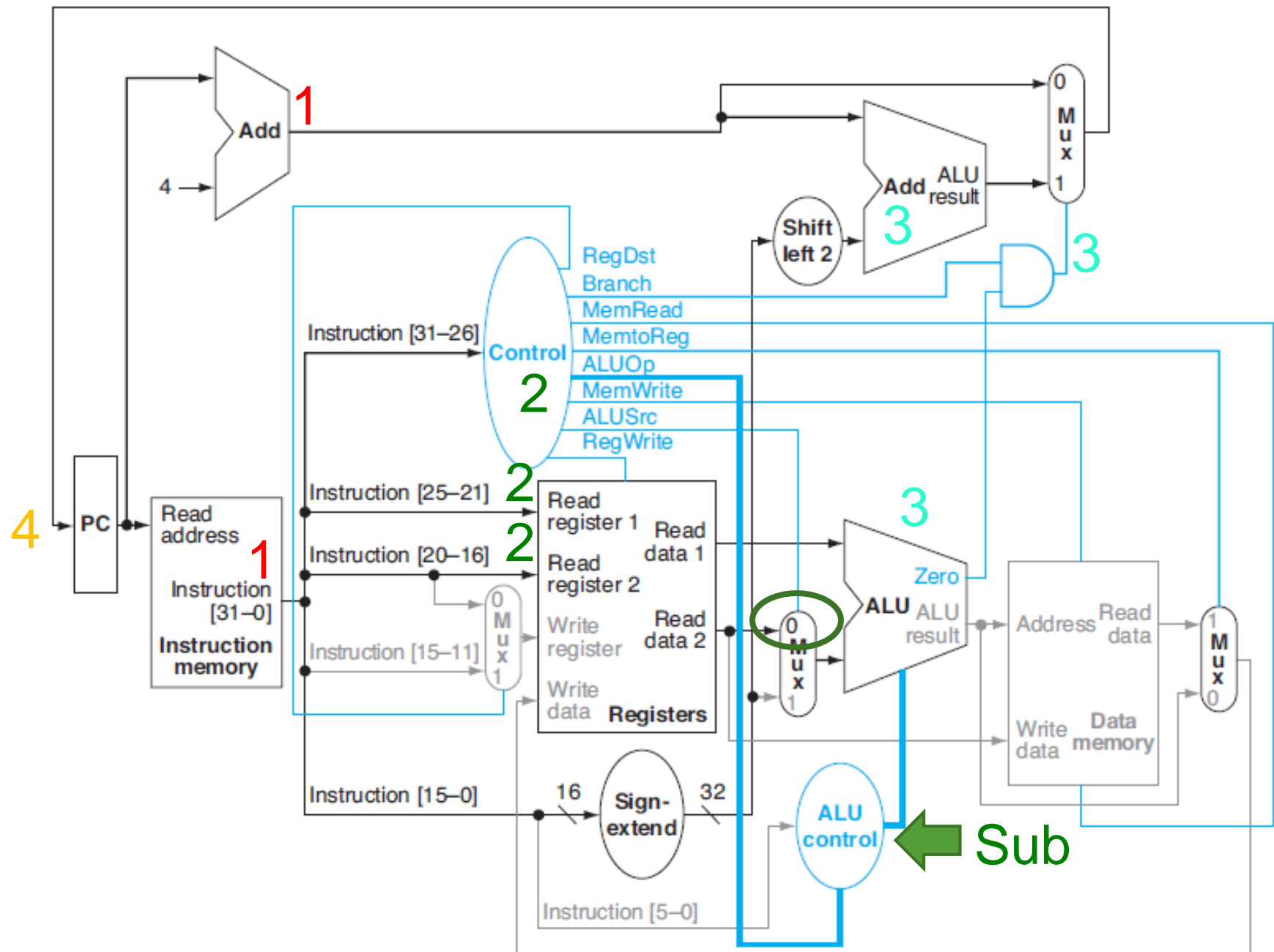1. An instruction is fetched from the instruction memory, and the PC is incremented.
2. Two registers, \$t1 and \$t2, are read from the register file.
3. The ALU performs a subtract on the data values read from the register file. The value of PC + 4 is added to the sign-extended, lower 16 bits of the instruction (offset) shifted left by two; the result is the branch target address.
4. The Zero result from the ALU is used to decide which adder result to store into the PC.



# Jump

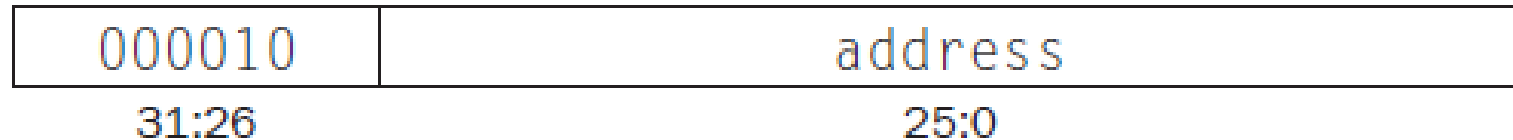

- we can implement a jump by storing into the PC the concatenation of
  - PC + 4
  - the 26-bit immediate field of the jump instruction
- One additional control signal is needed for the additional multiplexor.
- This control signal, called *Jump*, is asserted only when the instruction is a jump—that is, when the opcode is 2.

